

properties that make it particularly suited to our purpose, namely that it works at lower voltage levels than most other common diodes. Since the voltage in our radio comes from weak little radio waves, we need all the help we can get.

We now carry this diode in our [catalog](#), to make it easier to obtain. Radio Shack used to carry them, but they no longer have them in their stores.



We are now ready to build our simplest radio.

A very simple radio with two parts

First let me warn you that this first little radio may not work in your location. It relies on having a very strong local radio station to overcome the limitations of such a simple radio. If it does not work where you are, you can either build its cousins that we will discuss later, or you can drive out closer to a local radio station, and try it there. But because it is so simple, you might try building it just to see what you might be able to pick up.

If your earphone has a jack on the end, cut it off, so you have two long wires coming from the earphone. If the wires are twisted around each other, that is OK, since we only need them to be separate at the very ends.

Remove the covering (called insulation) from the ends of the wires to expose an inch of bare wire. Often you can do this with your fingernail, but a tool called a wire stripper is made for this purpose, and can usually be purchased at the same place you got the earphone or the diode.

Wrap one bare wire around one of the diode's wires. Use some tape to keep it in place. If you know how to solder, you can solder the wires together, but it really isn't necessary for now.



Tape the other diode wire to a cold water faucet. This makes a good connection to the ground, and is thus called a 'ground' connection.

Hold the remaining free bare wire of the earphone in your hand. This makes your body into the antenna for the radio. Put the earphone in your ear. If you are close to a strong AM radio station, you will be able to hear that station faintly in the earphone. You may hear more than one station at once.

If you can't hear anything, you might try a better antenna. You can tape the wire you were holding to a metal window screen, or a long wire. If one end of the long wire is thrown up on a roof or in a tree, you might get better results. Another good antenna is an outdoor TV antenna. Just touch the free earphone wire to one of the antenna terminals where it comes into the TV. If you have a good antenna, you may be able to eliminate the ground connection, using your body as a ground instead, by holding the free diode wire in your hand.

Another simple radio with two parts

Our simple radio has two main drawbacks. One is that the signals are very faint, and can only be heard if you are close to a radio station's transmitting antenna. The other is that you hear all of the strong stations at once, and it is hard to pick out just one song or voice from the mixed up jumble. The first problem is called the 'sensitivity' of the radio. Our radio is not very sensitive. The second problem is called the 'selectivity' of the radio. Our radio is not very selective.

We can solve both problems by using a trick called resonance.

Resonance is a way of taking a little bit of energy, and using it over and over again, at just the right time, to accomplish a big task. We use resonance when we push someone on a swing. It would take a lot of work

to lift someone several feet in the air, but we can do this easily on a swing by giving a little push over and over again at just the right time. Timing is important: if we push at the wrong time, the swing can actually lose energy instead of getting higher.

When an opera singer uses her voice to shatter a wine glass, she is using resonance. Her voice gives the glass a little push at just the right time, over and over again, until the glass is moving so far that it shatters. In a similar way, we can slosh all the water out of a bathtub by moving a hand in the water at just the right back and forth speed. Each time the hand moves, the water climbs a little higher, until it is over the top of the tub.

Radio waves can act like the sound waves of the singer's voice, or like the waves in the bathtub. Radio waves can cause electrons to move back and forth in a wire, just like the water in the tub. If the radio waves are moving back and forth at the right frequency, then the electrons in the wire will just be crowding towards one end of the wire when the radio waves start moving them back to the other side. Just like the water in the tub, the electrons will crowd higher and higher at the ends of the wire. These electrons can do work, like moving the brass disk in the earphone to create sound.

We can use resonance to build a radio that can pick up only one station at a time, and make a louder sound in the earphone. This radio will also have some drawbacks (for one thing it will be over 1,000 feet long!) but we will solve these problems in the next radio we build.

Suppose we pick a local radio station we want to hear. For this example we will choose 740 kilohertz on the AM dial. We now need to figure out how long the wire must be to resonate at this frequency. Radio waves travel at the speed of light. This radio wave is going back and forth 740,000 times per second. This means the wave needs to go about a quarter of a mile in one direction, then turn around and go back again, over and over. The actual formula for figuring out how long the wire should be is

936 feet

Frequency in Megahertz

or, for our example:

936 feet

.740

or about 1264 feet.


To make our radio, we take half of the wire (632 feet) and attach it to one end of the diode. We attach the other half of the wire to the other end of the diode. We attach one earphone wire to one side of the diode also, and the other earphone wire to the other end. We put the long wire up in the air by attaching each end to a tree (the trees must be about 1264 feet apart). Then we put the earphone into our ear, and listen to the radio.

Now I can think of a couple problems with this radio. It is not the most portable radio. Also, in order to change the station, we need to make the wire longer or shorter.


One solution to the portability problem is to coil the wire up by winding it on a box or a cylinder. Then we can solve the tuning problem by attaching the diode and earphone to the coil at different places (easy to do now that the whole wire is in one small place).

A simple radio with three parts

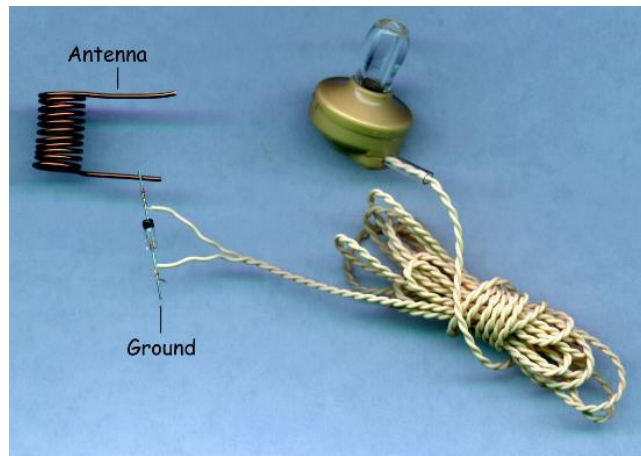There are several ways to connect a coil of wire to a diode and earphone to make a radio. In the photos below, we show two possibilities that work.



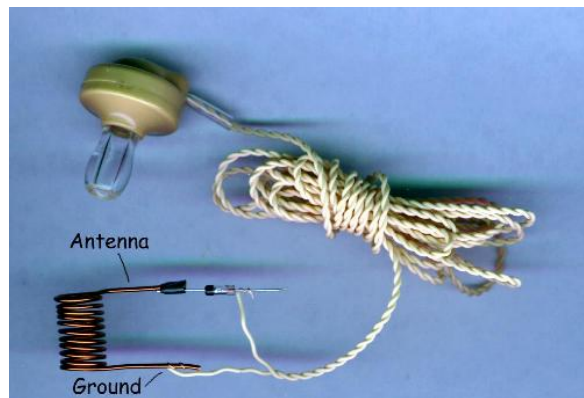
The photos do not show the antenna and ground connections, but instead indicate where they would be attached.



The coil in the photos is also dramatically simplified. A real coil for the AM radio frequencies would be somewhat larger, as we saw when we built our first radio using the plastic bottle.

Often photographs show so much detail that the important parts are easily missed. By using a simplified drawing, we can accentuate the important parts of the circuit and leave out unimportant or distracting details that can interfere with getting the point across.

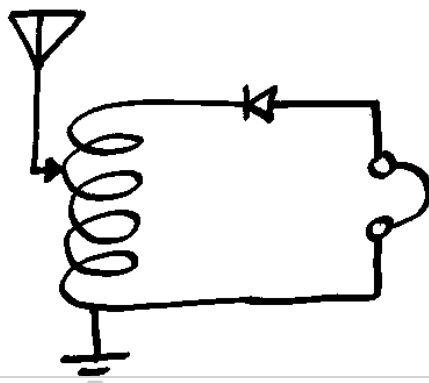A simplified drawing of a circuit is called a *schematic*. A schematic for a simple crystal radio might look like this if drawn on a napkin at a party:



The symbol for a coil looks like a spring. The symbol for an antenna looks like someone used a coat hanger. The symbol for headphones looks like the old fashioned ear-muff style (which are great for crystal radios, since they

block out ambient noise in the room). The symbol for the ground looks like what a cartoonist would draw under a cartoon character to represent the earth.

Note that the antenna is attached to the coil in the middle by a small arrow. This indicates that it is attached to a tap in the coil. An arrow is used to indicate a connection that can move, like our clip lead.

The symbol for the diode looks nothing like the little glass tube with wires coming out. Instead of representing what the diode *looks* like, it represents what the diode *does*.

A diode is a one-way valve for electricity. The electric current flows through the diode in one direction, but is blocked if it tries to flow in the other direction. We will find out why this is important later, when we learn why the radio works. But for now, we will concentrate on building a radio that will let us hear one station at a time, with reasonable loudness.

Power from radio waves -- hooking up a meter to measure the voltage and current

It is useful at this point to be able to measure the effects of changes we make to the radio. We can just use our ears and try to remember how loud it used to be, but it is easier to read a meter, and remember a number. With a meter connected to the radio we can adjust the tuning for the highest meter reading, or make other adjustments as we add new components or replace purchased components with ones we make ourselves.

The meters must be sensitive to very small changes in the amount of electricity flowing in our radio. We will be measuring *current* mostly, but we will add a voltmeter as well, so we can calculate the total amount of energy we are receiving.


Current is the flow of electricity through the circuit, and it is measured in amperes, or amps for short. Voltage is the pressure that pushes the current through the wires. If electricity were water, current would be the amount of water flowing (gallons per minute), and voltage would be the water pressure in pounds per square inch.

Since the amount of current is very small, we will use a meter that measures current in micro-amperes, or at most small fractions of a milliampere. Some examples of microammeters and milliammeters can be seen in the photo below:



To measure the current in our radio, we will need to have the current flowing through the meter. To do this, we connect the microammeter between the earphone and the ground connection, so that any electricity that is going to flow through the earphones to make noise is going to have to flow through the meter also. The meter can be connected in two ways, one is forward and one is backward. If the meter is connected backward, the needle will start reading below zero. If this happens, just reverse the connections, so the needle reads above zero.

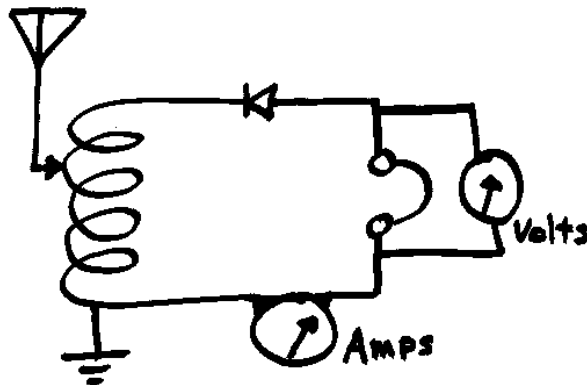To measure the voltage, we connect the meter to both of the earphone wires. The schematic diagram now looks like this:



If you have a good antenna, or a strong radio station nearby, the ammeter might read more than 50 microamps. If you have a short antenna, you might get only 5 microamps and still be able to hear the station clearly in the headphones. I put up a 200 foot antenna between two trees over my house, and tuned to a 50,000 watt station about 30 miles away, and now I get 175 microamps of current through my meter. I put the earphone to the mouth of a cone (like a megaphone) and I can clearly hear the radio from across the room when the house is quiet. It doesn't sound as nice and clear as it does with the earphone right up to my ear, but I can follow a conversation easily (it's an all-news station).

The voltmeter in the same radio reads 125 millivolts. Since watts (the measure of how much power we have) is the voltage multiplied by the amperes, we have 0.000175 times 0.125, or 0.0000218 watts, or about 22 microwatts. The station is putting out 50 kilowatts, and we are receiving one ten billionth of that power, yet we can hear it across the room.

Try different lengths of antenna, and watch the current go up as the longer antennas catch more of the power from the radio station. Try more than one antenna. Try connecting the ground wire to different things that are connected to the ground, such as pipes, metal fences, etc. As you try each test, make sure you tune the radio again, because your changes may affect the tuning.


Adding a capacitor (or three)

As you tried different antenna lengths, you may have noticed that you had to move the tap on the coil in order to get the station at its loudest. To understand why this happens, and how we can use an understanding of it to improve our radio, we must first understand *capacitance* and how it affects the tuning coil.

A capacitor is simply two pieces of metal with an insulator between them. If a capacitor is connected to a battery, the battery will push electrons onto one piece of metal (called a *plate*) and draw electrons from the other piece of metal. If we remove the battery, the electrons can't go anywhere, so one plate of the capacitor will have more electrons than the other plate.

If we connect the two plates together with a wire, the electrons will rush from the plate that had too many (because electrons have the same charge, and thus repel each other like the north poles of two magnets) to the plate that had fewer electrons. As the electrons rush from one plate to the other, we can make them do work, such as light a light bulb. In this way, the capacitor seems to store the electricity from the battery, for use at another time when the battery isn't there.

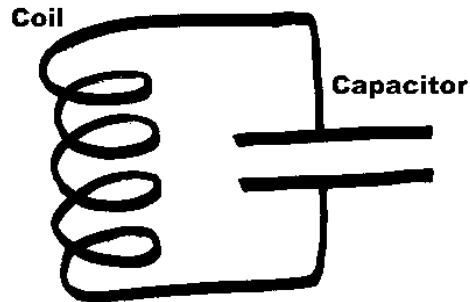Now suppose we connect a coil and a capacitor together like this:



Suppose also that the capacitor has been charged by a battery so the top plate has more electrons than the bottom plate. When we connect the coil, the excess electrons in the top plate immediately start traveling through the coil to get to the plate that has a shortage of electrons.

As the electrons travel through the coil, they create a magnetic field, (remember 'coil' is just another word for 'electromagnet'). The magnetic field grows until the plates on the capacitor have equalized. At this point you would think the current would stop flowing in the coil. But the magnetic field that built up when the current flowed through the coil now starts to collapse.

Just as moving a magnet past a coil will generate a current, a collapsing magnetic field around a coil creates a current too. The current is in the same direction as it was when the magnetic field was created, so the coil ends up pushing electrons onto the bottom plate of the capacitor, and stealing them from the top plate.

By the time the magnetic field around the coil has completely collapsed, the bottom plate of the capacitor has a surplus of electrons, and the top plate has a deficit. You can guess what happens next.

The electrons start flowing back into the coil, this time from the bottom plate to the top. The coil starts building up a magnetic field again, but since the current is now going the other way, what used to be the north pole of the magnetic field is now the south pole, and vice-versa.

The field grows until the capacitor has equalized, then it collapses, and pumps electrons into the top plate of the capacitor. We are now back where we started, and the whole process starts over again!

The coil and the capacitor are resonating, just like the child on a swing, or the water in a bathtub. In fact, this circuit is called a 'tank circuit', like a tank full of water that sloshes back and forth.

We can control the frequency of the oscillations in two ways. We can make the coil larger or smaller, or we can make the capacitor larger or smaller. The coil we built for our radio has taps, which have the effect of making the coil shorter or longer, depending on which tap we connect to the antenna.


Our radio has a coil. But it doesn't have a capacitor. Or does it? Actually, the antenna itself is acting like a capacitor. The capacitance of the antenna is reacting with the *inductance* of the coil to resonate at the frequency of the radio station.

When we change the length of the antenna, it is like changing the size of the capacitor. This is why changing the length of the antenna changed the tuning of the radio, forcing us to move to a different tap on the coil in order to listen to the same station.


There is another way to change the capacitance of a capacitor. We can change the distance between the two plates. If the plates are closer together, the excess electrons on one plate are attracted to the other plate, because when the negatively charged electrons were removed from that plate, it was left with a positive charge.

Because the electrons are attracted to the positive charge, we can pile more of them together, storing more energy. In a similar fashion, when we make a capacitor with the plates farther apart, the positive charge is farther away, and can't help to pull as many electrons onto the negative plate. Thus the amount of energy we can store is less, and we say the capacitor has less *capacity*.

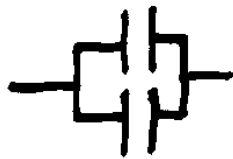We can combine capacitors to raise or lower the capacitance, now that we know how capacitors work. If we put two capacitors together in parallel, we can increase the capacitance, because the top plates are connected together, and the bottom plates are connected together, it is just as if we had one capacitor with large plates.




If we connect the capacitors in series, it has the effect of making the plates of the capacitor be farther apart. This can be seen in the illustration below. The bottom plate of one capacitor is connected to the top plate of the other. Electrically, this is the same as making the two plates into one plate in the middle of a capacitor that has twice the distance between the outer plates. The phantom inner plate has no effect, and is drawn as a dotted line in the bottom illustration.

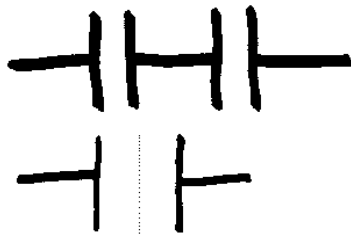

We now know enough about capacitors to use them in our radio. We can use a small capacitor between the antenna and the coil to lower the capacitance of the antenna. This will allow the coil to tune to stations that are higher in frequency. The capacitor is in series with the capacitance of the antenna, so the total capacitance is lower.

The circuit now looks like this:

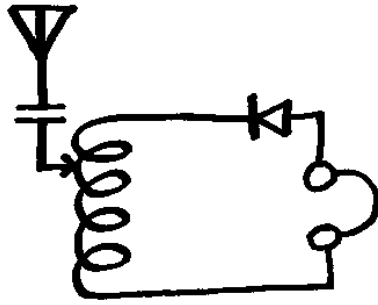

Building your own capacitors


Capacitors are easy to build in the kitchen out of aluminum foil. In fact, our first capacitor will simply be two sheets of foil tucked into a paperback book, with one page separating them, as if they were two bookmarks.



This quick capacitor has advantages and disadvantages. It is quick and easy to build, it can be easily adjusted to vary the capacitance by simply sliding one of the foil strips out of the book a little at a time, thus reducing the capacitance. On the other hand, it is bulky, and comes apart easily, and will change its capacitance when you press down on the book, squeezing the pages closer together. Lastly, it can change capacitance slightly on humid days as the pages of the book absorb moisture.

With only a little more effort, we can make a durable, stable, capacitor using foil and a little waxed paper or plastic wrap.


We start by laying down a sheet of waxed paper. On top of that we lay a sheet of foil. We leave the foil hanging over the top of the waxed paper, so we will have something to which we can attach a wire. We lay another piece of waxed paper over the first piece and the foil. We then lay another piece of foil on the top, overlapping it at the bottom for our other wire. We make sure that the foil sheets are always separated by the waxed paper, so they do not make an electrical connection.

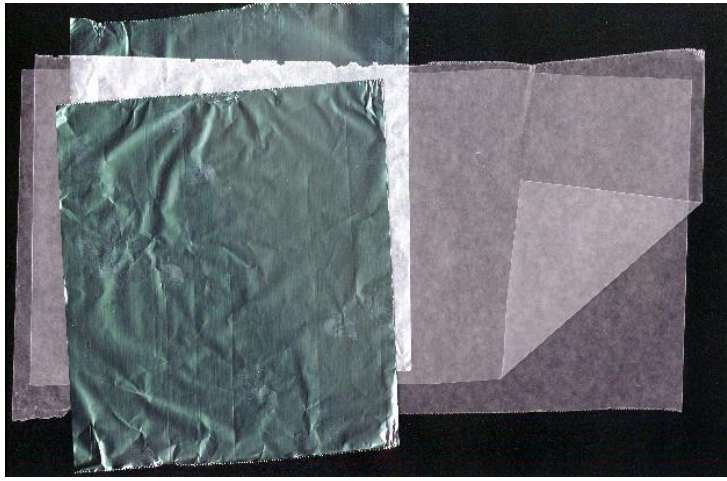

Now we roll the whole thing up like a jelly roll.



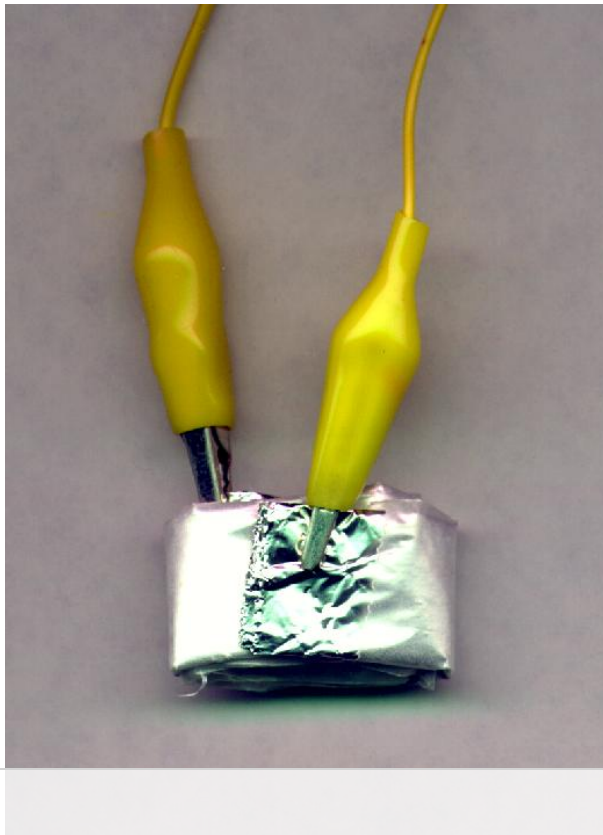
Now we trim up the paper with some scissors, and we can even roll it up the other way to make it smaller.



This capacitor is not adjustable like our first one, but we can make several of them, each a different size, and connect the one we want. We can even combine them in parallel or in series to change their capacitance.

We can use the small *fixed* capacitor to tune the antenna, and another *variable* capacitor (like our book capacitor) to tune the coil. We put the variable capacitor in parallel with the coil, to make a tank circuit. The small fixed capacitor lowers the antenna's capacitance, making the circuit tune to a higher frequency. But the variable capacitor adds more capacitance to the circuit, making it tune to a lower frequency. Now we can tune the radio with the taps on the coil, *and* by sliding the foil in and out of the book.

The circuit now looks like this:

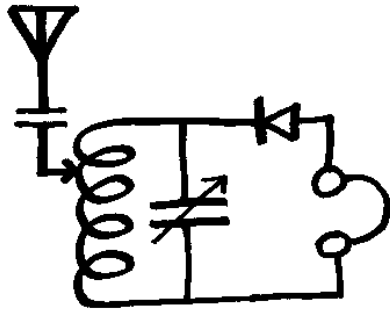

Notice how the variable capacitor has an arrow through it to indicate that it can change its capacitance.


Building your own diodes

During World War I, soldiers in the field made their own radios to listen to programs for entertainment and news. They had access to wire from broken down vehicles, and telephone receivers, but they did not have modern solid state diodes in little glass tubes.


However, it is surprising to find out just how many ordinary objects can act as a diode, letting current flow one way better than another.

The soldiers found that an old rusty razor blade and a pencil lead worked just fine. By lightly touching the pencil lead to spots of blue on the blade, or to spots of rust, they formed what is called a *point contact* diode.

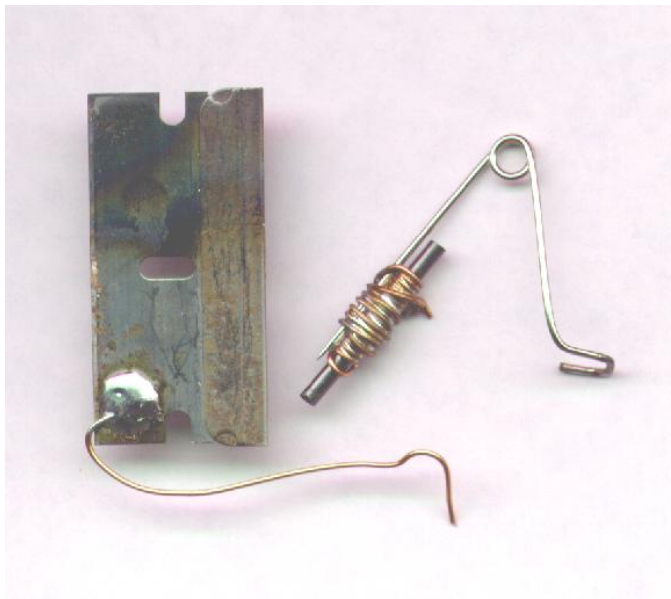We can replace our store-bought diode with a homemade point contact diode and compare the results. The parts can be attached to the circuit with clip leads, or they can be soldered, as in the photo below. The pencil lead is attached to a safety pin by wrapping it with bare copper wire and soldering it.



The safety pin acts as a spring to lightly press the pencil lead onto the razor. If the pressure is too hard or not hard enough, the diode will not work, so experiment. The exact spot on the razor is also critical, since some spots will have too much or too little oxide on them to make the diode. Move the pencil lead around on the razor until the sound is loudest, or the meter (if you have attached one) reads highest.

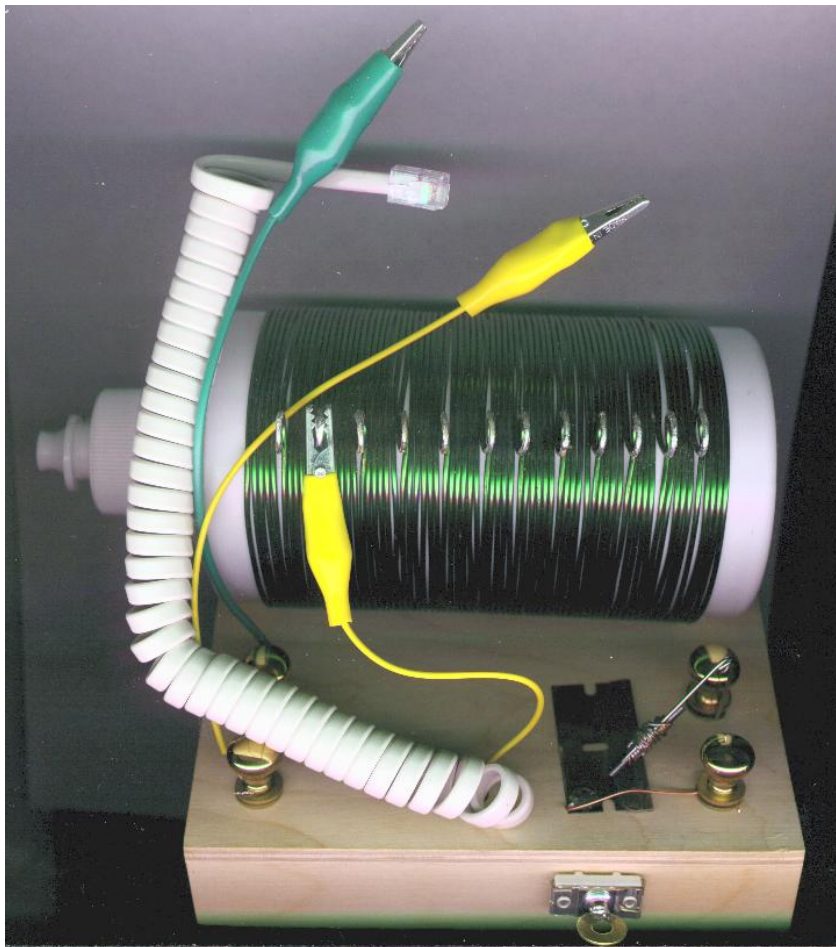

In the photo above, you can see how handy the brass drawer pulls are when we want to attach new types of diodes.

If you don't have a rusty razor blade lying around, you can try other bits of rusty metal. The blade shown above was clean and new, so I put a little

salt and water on it, and held it in the flame of a gas stove until parts of it were blue and purple.

You might have other things around the house that can act as diodes. In my rock collection, I found some iron pyrite (fool's gold) and some carborundum (silicon carbide, the blue stone in the photo below). The carborundum works well with a strong pressure, so I simply wrapped some bare copper wire around it, soldered the wire, and then let the jaws of a clip lead supply the pressure. It works quite well. The pyrite needs a gentle touch, so I used the point of a safety pin to gently probe until I found a spot on the pyrite that gave good volume in the radio.



Going further - some quick thoughts

Trading loudness for more stations

In our radio, the diode and earphones are connected directly to the antenna and ground. This connection gets the loudest signal. However, it also *loads* the tuning coil, making it less selective. This means that many lower power or distant stations are drowned out by local strong stations.

We can make the radio more selective by decoupling the tuning coil from the antenna and ground. We do this by adding a small coil. The new coil is attached to the antenna and the ground, and then it is placed inside the main tuning coil.

Wind about five or ten turns of wire around a small coil form such as the plastic container use to package 35 mm film (about 1 inch in diameter). Cut a large hole in the bottom of the plastic bottle on which we wound the large tuning coil. Attach the antenna and ground to the small coil, and